Comparison of the 3 adder designs

| Design | Critical Path Delay | Hardware Requirements | | | | |
|------------------------------|--------------------------------------------|-----------------------|-------------------------------------|------------------------------|-------------------------|------------------------------------------------------|
| Ripple Carry Binary Adder | ' ' ' ' ' ' ' ' ' ' ' ' ' ' ' ' ' ' ' ' | | Resource LUT | Post-Synth Utilization 8 | G Available 63400 | raph Table Utilization % 0.01 |
| Hybrid Binary Adder | =Max(delays of all paths) = 7.118 ns | Ut | IO Resource LUT IO | Post-Synth Utilization 8 26 | | nplementation raph Table Utilization % 0.01 12.38 |
| Bit-serial Binary Adder | =Max(delays of all paths) = 4.090 ns | Uti | Resource LUT FF IO BUFG | Utilization 69 54 27 | | 0.04 |